 


- 4) Consider for example the inputs are $J=K=1$ & $Q=0$ & pulse as shown in figure below is applied at clock input



After a time interval Δt equal to propagation delay in 2 NAND gates in series, the output will change to $Q=1$. Now, we have $J=K=1$ & $Q=1$ & after another time interval of Δt , the output will change back to 0. Hence we conclude that the value of Q will oscillate from 1 to 0 & between 1 & 0. This is called race around condition.


This condition can be avoided if $t_p < \Delta t < T$. However, it may be difficult to satisfy this inequality because of very small propagation delay in IC. To overcome this, we use Master-Slave JK flip flop.

A Master slave J-K flip flop is cascade of 2 J-K flip flop with feedback from the output of the second to inputs of first. Positive clock pulse are applied to the first flip flop & the clock pulses are inverted before being applied to the second. ~~when J=K=1~~

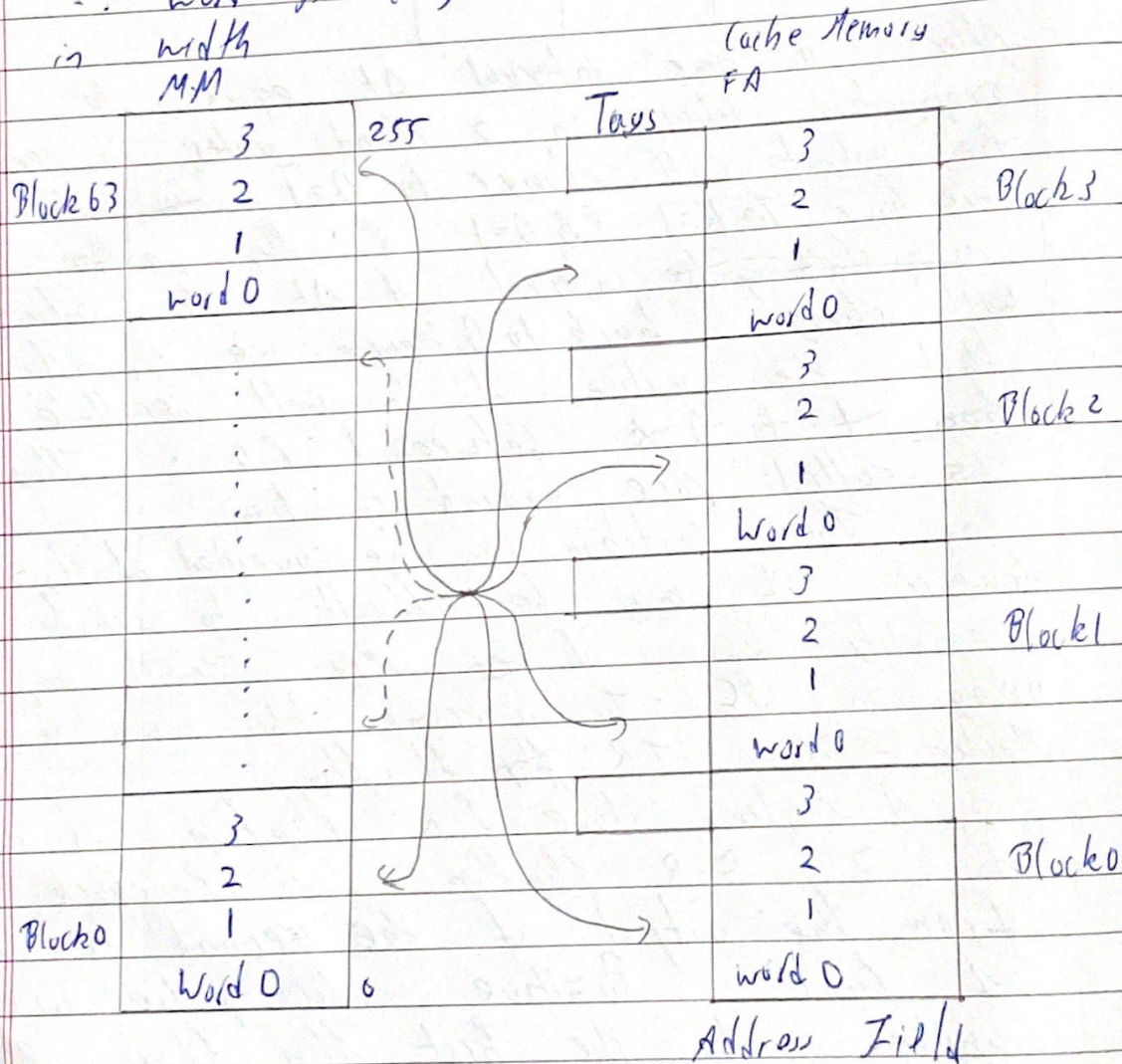3) Cache Memory of 16 Words - Each block consists of 4 words

Therefore, the cache memory is organized as 4 block of 4 words each

\therefore word field (W) is of $2^2 = 4 \rightarrow 2$ bits in width MM



T	W
Tag	Word
Field	Field
6 bit	2 bit

The ~~for~~ Main Memory is of 256 bytes.

119A1076

classmate

Date _____

Page _____

Total address field is of 8 bits.

However, Address field (A) = Tag field (T) + Word field (W) from

\therefore Tag field is associative

$$T = A - W = 8 - 2 = 6 \text{ bit}$$

The Main Memory is divided into 64 block and cache would be organised as 4 word of 4 block each. Any cache block can be populated to/from any block in MM